

Simple and Accurate High Side Current Sense Circuit

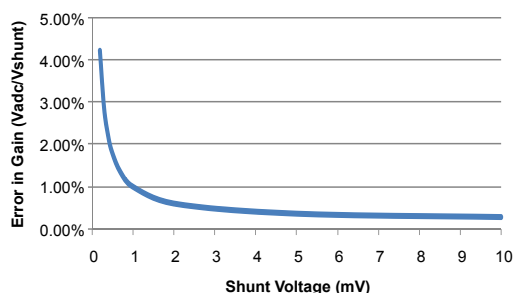


Figure 3: Error in gain (V_{adc}/V_{shunt}) assuming 0.1% resistors

Error in the current sense circuit of Figure 2, assuming 0.1% resistors and 8 μ V offset. Error due to the bias current of the ISL28133 (300pA) and leakage of Q3 is assumed insignificant.

Figure 3 shows the accuracy at room temperature for a typical sense voltage. This level of accuracy is acceptable in many cases. Obviously, there will be additional error over temperature. The circuit can be made much more accurate if needed. The current measurement is calibrated at room temperature in many applications, making the accuracy a function of the temperature drift only. Figure 4 shows the accuracy assuming calibration at room temperature using 10ppm/C resistors and a premium chopper amp, the ISL28134, which has an offset drift of 15nV/°C. Better than 0.2% precision is maintained down to a sensed voltage of 1mV.

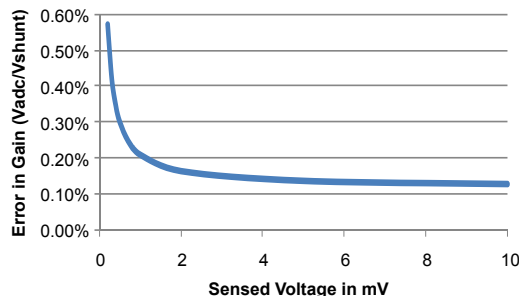


Figure 4: Error in gain (V_{adc}/V_{shunt}) over +/-60°C assuming 10ppm resistors, ISL28134 op amp and room temp calibration

Accuracy of the sense network over temperature (-40°C to +80°C) assuming room temperature calibration and using a premium grade amplifier ISL28134.

Stability and Bandwidth

Note that the manner in which the buffer transistor is configured should not destabilize the amp if the amp is internally compensated to be unity gain stable. The source of the buffer transistor Q3 follows the output of the amp and this buffering is therefore the equivalent of taking the output back to the inverting input, as in a unity gain configuration.

Another important item to note is that the buffer transistor Q1 does relieve the gain-bandwidth restrictions of the op

amp. The configuration in Figure 2 has a gain (V_{adc}/V_{shunt}) of $R7/R9=100$ from V_{shunt} to the output. Figure 5 shows the simulated frequency response of this circuit using the ISL28133. The gain-bandwidth of the amp is 400kHz, yet the overall circuit gain bandwidth is 100*200kHz or 20MHz. The buffer transistor improves the circuit bandwidth without destabilizing the op amp. The improvement in gain bandwidth is intuitive when viewed in this manner: With an input signal of 1mV and an ideal buffer transistor (i.e., one in which the gate-source threshold voltage is constant regardless of drain current), the output of the amp will only have a 1mV signal. So the op amp is functioning with an ac gain of 1. The voltage gain of 100 is achieved by the buffer transistor. With a non-ideal transistor, the output of the amp will have a somewhat higher signal (~2mV in this case), but the BW of the overall circuit is still ~half of the unity gain bandwidth of the amp and the gain-bandwidth of the circuit is ~50x the GBW of the op amp.

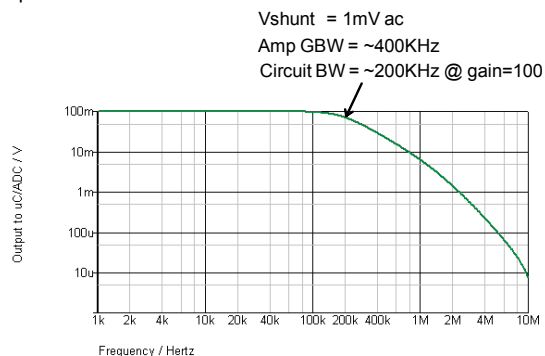


Figure 5: Frequency response of the circuit in Figure 2. 1mV input is applied at V_{shunt} and the output is measured V_{adc} . Note that the gain-Bandwidth of the overall circuit is 20MHz.

Summary

Accurate high side current sensing can be achieved using a low voltage, low offset op amp, combined with a simple, low power bias scheme and a level shift transistor. This approach can be lower cost and much more accurate than circuits requiring higher voltage amplifiers. When sensing a 10mV signal, room temperature, full scale accuracy of <0.3% is achieved with 0.1% resistors and the ISL28133 chopper stabilized amplifier. With the ISL28134 and room temperature calibration, 0.2% is maintained over temperature with 1mV sensed. The circuit topology is inherently stable, yet the gain bandwidth of the overall circuit is significantly higher than that of the op amp by itself. In the example, the gain bandwidth of the overall circuit is improved by a factor of 50.

Reference Documents

- Intersil "High-Side, Current Sensing Techniques" App Note: AN1827

Sensor: shunt, low ohmic, hall effect, resistor, high side, low side, bi-directional, flow sensor

Applications: power monitor, voltage monitor, current monitor, industrial controls, instrumentation, medical, portable, battery monitor, data loggers, 4-to-20mA current loops, energy harvesting, wireless solution, overcurrent, undercurrent, fault detection, motor control, remote sensing, power management, energy meters, wind power, alternative energy, Servers, cloud computing, microservers, telecom, mobile radio, inductive charging, enterprise switch, BST, smart phones, LCD Display Tablet/PC, distributed power, basestations, power supplies, networking, inverters, solar, negative voltage monitor, -48V supplies, rack mount power, power strip, surge protection, PLC, smart power

Performance: high performance, low power, micro power, high voltage, low cost, precision analog, signal conditioning, 16-bit Sigma Delta, zero-drift, chopper, chopper stabilized, low offset drift, low noise